

# Task 1: Full Adder

## Part 1.1: Derive the logic for a 1-bit adder

Truth Table:

CI	B	A	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Boolean Logic:

**Carry Over Bit:**

$$CO = A B \bar{CI} + A \bar{B} CI + \bar{A} B CI + A B CI$$
$$CO = A B (CI + \bar{CI}) + \bar{A} B CI + A \bar{B} CI = A B + \bar{A} B CI + A \bar{B} CI$$
$$= A(\bar{B} CI + B) + \bar{A} B CI = A (CI + B) + \bar{A} B CI$$
$$= A CI + A B + \bar{A} B CI = A B + CI(\bar{A} B + A)$$
$$= A B + CI (B + A) = A B + B CI + A CI$$

**Sum Bit:**

$$S = A \bar{B} CI + \bar{A} B \bar{CI} + \bar{A} B CI + A B CI$$
$$= A \oplus B \oplus CI$$

## Part 1.2: Implement the 1-bit adder

```
module FullAdder(input a, input b, input ci, output s, output co);
    /*
    Implement a full adder using verilog
    */
    /*
```

```

using data flow modeling
assign s = a ^ b ^ ci;
assign co = (a & b) | (b & ci) | (a & ci);
*/
wire tempSum;
wire foo;
wire bar;
wire baz;
wire quux;


xor(temp, a, b);
xor(s, temp, ci);

and(foo, a, b);
and(bar, b, ci);
and(baz, a, ci);
or(quux, foo, bar);
or(co, baz, quux);

endmodule

```

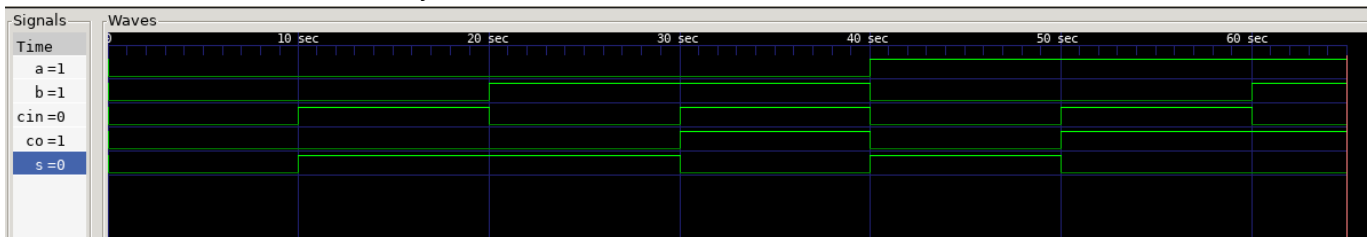Used a testbench to test the values for each value of a, b, and ci with a #10 delay. Here is the GTKWave screenshot, and test.vcd is here if you want to use a waveform viewer.



### Part 1.3: Using the 1bit adder, implement a 4 bit adder


```

module FourBitAdder(input [3:0] a, input [3:0] b, output [4:0] s);
/*
implement a 4 bit adder using full adder from above
*/
wire [2:0] c;
FullAdder first(a[0], b[0], 1'b0, s[0], c[0]);
FullAdder second(a[1], b[1], c[0], s[1], c[1]);
FullAdder third(a[2], b[2], c[1], s[2], c[2]);
FullAdder fourth(a[3], b[3], c[2], s[3], s[4]);

endmodule

```

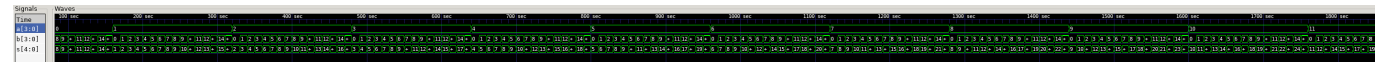I created a testbench using a loop from 0 to 255 to assign the value to both inputs and used gtkwave to confirm that each value was correctly assigned. test\_four.vcd is the filename for waveform simulation



# Task 2: 7 Segment

## Part 2.1: Convert a binary number to 7-segment display encoding

Display	S3	S2	S1	S0	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	1	1	0	0	1	1	1	0
2	0	0	1	0	0	0	1	0	0	1	0
3	0	0	1	1	0	0	0	0	1	1	0
4	0	1	0	0	1	0	0	1	1	0	0
5	0	1	0	1	0	1	0	0	1	0	0
6	0	1	1	0	0	1	0	0	0	0	0
7	0	1	1	1	0	0	0	1	1	1	1
8	1	0	0	0	0	0	0	0	0	0	0
9	1	0	0	1	0	0	0	0	1	0	0
A	1	0	1	0	0	0	0	1	0	0	0
B	1	0	1	1	1	1	0	0	0	0	0
C	1	1	0	0	0	1	1	0	0	0	1
D	1	1	0	1	1	0	0	0	0	1	0
E	1	1	1	0	0	1	1	0	0	0	0
F	1	1	1	1	0	1	1	1	0	0	0

## Part 2.2: 7-Segment Display

```
module SevenSegment(input [3:0] a, input [3:0] b, output [6:0] d, output
overflow);
    reg [6:0] d;
    wire [4:0] s;
    wire [3:0] lessSig;

    FourBitAdder add(a, b, s);
    assign overflow = s[4];
    assign lessSig = s[3:0];

    always @(lessSig) begin
        case (lessSig)
```

```

0 : d = 7'b0000001;
1 : d = 7'b1001110;
2 : d = 7'b0010010;
3 : d = 7'b0000110;
4 : d = 7'b1001100;
5 : d = 7'b0100100;
6 : d = 7'b0100000;
7 : d = 7'b0001111;
8 : d = 7'b0000000;
9 : d = 7'b0000100;
10 : d = 7'b0001000;
11 : d = 7'b1100000;
12 : d = 7'b0110001;
13 : d = 7'b1000010;
14 : d = 7'b0110000;
15 : d = 7'b0111000;

endcase
end

endmodule

```


Used a similar testbench to the FourBitAdder, with code in SevenSegment\_tb.v where each value for the less significant digits are assigned to a binary according to the truth table above. Image for simulation below.



## Task 3: Finite State Machine

### Part 3.1: Design the FSM

(i) Draw the State Diagram

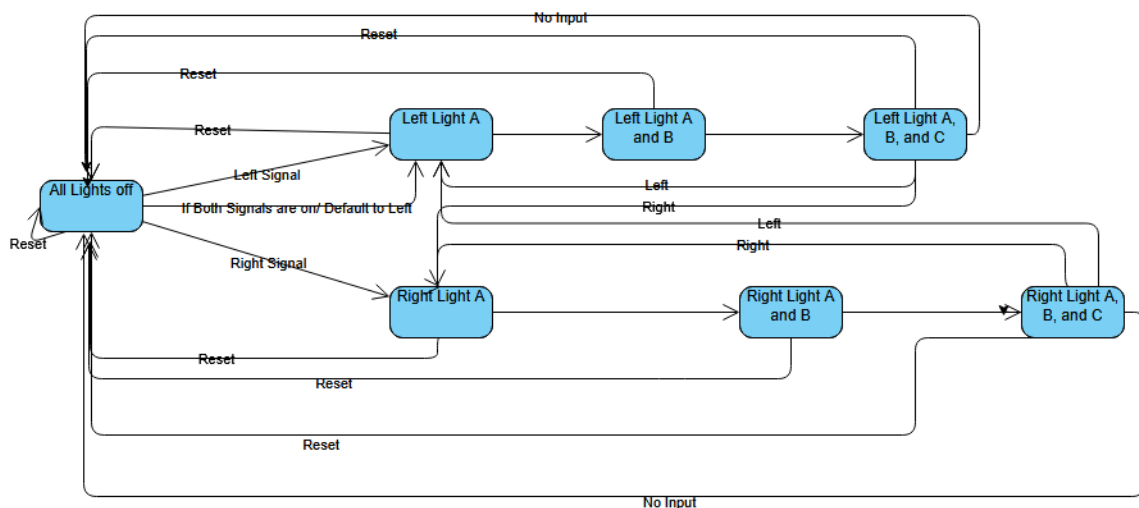

(ii) Draw a table describing the states to binary values

state	binary value
init	0000
RA	0001
RAB	0011
RABC	0111
LA	1000
LAB	1100
LABC	1110

(iii) How to map binary state value to outputs

state	binary value	Output signals
init	0000	000000
RA	0001	001000
RAB	0011	011000
RABC	0111	111000
LA	1000	000100
LAB	1100	000110
LABC	1110	000111

## Part 3.2: Implement the FSM

```

module TailLight(input rst, input clk, input l, input r,
output reg lc, output reg lb, output reg la,
output reg ra, output reg rb, output reg rc);

    reg [3:0] state, nextState;

    // various states
    parameter INIT = 4'b0000;
    parameter RA = 4'b0001;
    parameter RAB = 4'b0011;
    parameter RABC = 4'b0111;
    parameter LA = 4'b1000;
    parameter LAB = 4'b1100;
    parameter LABC = 4'b1110;

    // handle state register update on clock cycle
    always @ (posedge clk) begin

```

```
    if(rst)
        state <= INIT;
    else
        state <= nextState;
    end

// next state logic
always @(*) begin
    case(state)
        INIT:   nextState = 1 ? LA : r ? RA : INIT;
        RA:     nextState = RAB;
        RAB:    nextState = RABC;
        RABC:   nextState = 1 ? LA : r ? RA : INIT;
        LA:     nextState = LAB;
        LAB:    nextState = LABC;
        LABC:   nextState = 1 ? LA : r ? RA : INIT;
        default:nextState = INIT;
    endcase
end

// Output logic
always @(*) begin
    case(state)
        INIT: begin
            lc <= 0;
            lb <= 0;
            la <= 0;
            ra <= 0;
            rb <= 0;
            rc <= 0;
        end
        RA: begin
            lc <= 0;
            lb <= 0;
            la <= 0;
            ra <= 1;
            rb <= 0;
            rc <= 0;
        end
        RAB: begin
            lc <= 0;
            lb <= 0;
            la <= 0;
            ra <= 1;
            rb <= 1;
            rc <= 0;
        end
        RABC: begin
            lc <= 0;
            lb <= 0;
            la <= 0;
            ra <= 1;
            rb <= 1;
            rc <= 1;
        end
    end
end
```

```

end
LA: begin
    lc <= 0;
    lb <= 0;
    la <= 1;
    ra <= 0;
    rb <= 0;
    rc <= 0;
end
LAB: begin
    lc <= 0;
    lb <= 1;
    la <= 1;
    ra <= 0;
    rb <= 0;
    rc <= 0;
end
LABC: begin
    lc <= 1;
    lb <= 1;
    la <= 1;
    ra <= 0;
    rb <= 0;
    rc <= 0;
end
default: begin
    lc <= 0;
    lb <= 0;
    la <= 0;
    ra <= 0;
    rb <= 0;
    rc <= 0;
end
endcase
end
end

endmodule

```

I wrote a testbench that tests various cases, including reset in the middle of a cycle, both inputs being on at the same time, and if states can be consecutively swapped between each other. Below is a screenshot of GTKWave and the full code for the testbench is in TailLight\_tb.v I was struggling initially to get the outputs driven in the TailLight.v, so I changed all the outputs to register types. I am still looking into how to do this with wires instead.

